

Traffic Lights

Parallel or Series Circuit?

Open or closed circuit?

Where is the switch?

